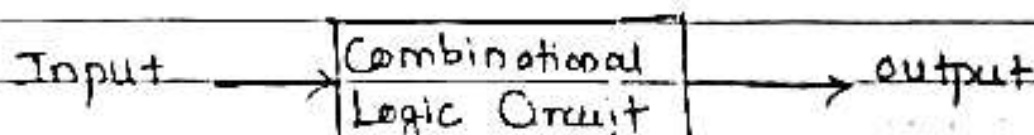


# Unit No. 3 Combinational Logic Design

Page No.	
Date	

A combinational logic circuit is a circuit whose output depends only on the present input values, not on past inputs (no memory element).

eg. Adders, subtractors, Multiplexers, Demultiplexers, encoders, decoders.



## General Characteristics

- It doesn't have feedback element (i.e. output not fed to input.)
- Output is determined by a logic expression of inputs.
- These are represented using Boolean functions.

## Standard Representations for logic functions

### a) Boolean function

A Boolean function maps binary input values (0 or 1) to a binary output.

eg.  $Y = \bar{A}B + A\bar{B}$

### b) Truth table

It is a Tabular form listing all input combinations and their corresponding outputs.

## 2) Product of sum (POS)

It is a unique, standard Boolean expression where each sum term (a maxterm) contains every variable of the function, and the entire expression a product of these maxterms.

It's derived from truth table by identifying the rows where the output is 0.

Forming a maxterm for each (a sum of the complemented variable if the input is 0, and the uncomplemented variable if the input is 1) and then logically ANDing these maxterms together.

lets learn how to write POS form with an example consider the following truth table.

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

• Identify maxterms for o/p '0'.

look for the rows where the function's output Y is '0'.

∴ A, (0, 0, 1), (0, 1, 0), (1, 0, 1)

Don't care condition in k-map

- In digital design, some input conditions never occur or the output doesn't matter for those cases.

Instead of fixing them as 0 or 1, we mark them as X (don't care)

In simplification  $\rightarrow$

we can use them as 1's (for SOP minimization)

Or use them as 0's (for POS minimization)

or ignore them if they don't help.

- SOP example with Don't care

$$F(A, B, C) = \sum (1, 2, 7) + d(0, 3)$$

1 at minterms  $m_1, m_2, m_7$

Don't care at  $m_0, m_3$

Plot k map  $\rightarrow$  (3 variables)

AB \ C	0	1
00	X( $m_0$ )	1( $m_1$ )
01	1( $m_2$ )	X( $m_3$ )
11	0	1( $m_7$ )
10	0	

use  $m_0, m_1, m_2, m_3 \rightarrow$  group of 4  $\rightarrow$  gives  $A'$

use  $m_2, m_7 \rightarrow$  group of 2  $\rightarrow$  gives BC

Final expression  $\rightarrow F = A' + BC$

POS example with d Don't care

$$F(A,B,C,D) = \Pi(0,1,2,3,8,9) + d(10,11)$$

Mark 0's and X's

0's at minterms 0, 1, 2, 3, 8, 9

X's at minterms 10, 11

Grouping

use X's and 0's to form larger groups.

4x4 Kmap

AB\CD	00	01	11	10				
00	m <sub>0</sub>	m <sub>1</sub>	m <sub>3</sub>	m <sub>2</sub>	0	0	0	0
01	m <sub>4</sub>	m <sub>5</sub>	m <sub>7</sub>	m <sub>6</sub>	1	1	1	1
11	m <sub>12</sub>	m <sub>13</sub>	m <sub>15</sub>	m <sub>14</sub>	1	1	1	1
10	m <sub>8</sub>	m <sub>9</sub>	m <sub>11</sub>	m <sub>10</sub>	0	0	X	X

Top row (m<sub>0</sub>, m<sub>1</sub>, m<sub>2</sub>, m<sub>3</sub>) - one group of 4

Bottom-left (m<sub>8</sub>, m<sub>9</sub>, m<sub>10</sub>, m<sub>11</sub>) - another group of 4 (including don't cares at m<sub>10</sub>, m<sub>11</sub>)

- Expressions from groups.

group 1 (m<sub>0</sub>-m<sub>3</sub> entire top row)

AB = 00 (so A=0, B=0 → A'B')

CD varies → eliminated.

In POS form, row of 0's → factor = (A+B)

group 2 (entire bottom row m<sub>8</sub>, m<sub>9</sub>, m<sub>10</sub>, m<sub>11</sub>)

AB = 10 (so A=1, B=0 → AB')

CD is 00-11 range, but we use X's eliminated.

so group factor = (A'+B)

$$\therefore F = (A+B)(A'+B)$$



## 4 Variable k-map

16 cells (A, B across top, C, D along side)

AB \ CD	00	01	11	10	or			
00	F <sub>0</sub>	F <sub>1</sub>	F <sub>3</sub>	F <sub>2</sub>	m <sub>0</sub>	m <sub>1</sub>	m <sub>3</sub>	m <sub>2</sub>
01	F <sub>4</sub>	F <sub>5</sub>	F <sub>7</sub>	F <sub>6</sub>	m <sub>4</sub>	m <sub>5</sub>	m <sub>7</sub>	m <sub>6</sub>
11	F <sub>12</sub>	F <sub>13</sub>	F <sub>15</sub>	F <sub>14</sub>	m <sub>12</sub>	m <sub>13</sub>	m <sub>15</sub>	m <sub>14</sub>
10	F <sub>8</sub>	F <sub>9</sub>	F <sub>11</sub>	F <sub>10</sub>	m <sub>8</sub>	m <sub>9</sub>	m <sub>11</sub>	m <sub>10</sub>

Gray code order is used for columns (00, 01, 11, 10) and rows (00, 01, 11, 10)

### Minterms (SOP)

example  $m_0 = A'B'C'D'$

$m_1 = A'B'C'D$

$m_{15} = ABCD$

### 1) SOP example

$$F(A, B, C, D) = \sum (0, 2, 8, 10)$$

Plot 1's in k-map

place 1 at  $m_0, m_2, m_8, m_{10}$

these cells form a rectangle of 4

$m_0 = 0000 \Rightarrow A=0, B=0, C=0, D=0$

$m_2 = 0010 \Rightarrow A=0, B=0, C=1, D=0$

$m_8 = 1000 \Rightarrow A=1, B=0, C=0, D=0$

$m_{10} = 1010 \Rightarrow A=1, B=0, C=1, D=0$

Observe constants across all four minterms

$B=0$ , and  $D=0$

A and C vary

$\therefore B = B'D'$

Form maxterms

$$(0, 0, 1) \rightarrow A+B+C'$$

$$(0, 1, 0) \rightarrow A+B'+C$$

$$(1, 0, 1) \rightarrow A'+B+C'$$

And the maxterms  $\rightarrow$

$$Y = (A+B+C') \cdot (A+B'+C) \cdot (A'+B+C')$$

K-Map representation for logic function  
(K-map  $\rightarrow$  Karnaugh map)

- It is a graphical method for simplification of Boolean function.
- Advantages - Reduces complex expressions  
easy visualization  
helps minimize gates.
- A K-map is a truth table arranged in a special 2D form.
- Adjacent cells differ in only one variable (Gray code Order)
- Group size must be a power of 2 (1, 2, 4, 8...etc)

2 Variable K-map

- Two input variables  $\rightarrow 2^2 = 4$  minterms
- The K-map has 2 rows  $\times$  2 columns = 4 cells.

A \ B	0 (B=0)	1 (B=1)	
0	$m_0$	$m_1$	$m_0 = A'B$
1	$m_2$	$m_3$	$m_1 = A'B$
			$m_2 = AB'$
			$m_3 = AB$

Simplify further

$$\begin{aligned} F &= (A+B)(A'+B) \\ &= (AA' + AB + A'B + BB) \\ &= (0 + AB + A'B + B) \\ &= AB + A'B + B \\ &= B + (AB + A'B) \end{aligned}$$

$$\boxed{F = B}$$

## POS example

Solve

$$F(A, B, C, D) = \Pi(1, 3, 9, 11)$$

that means the function is 0 at minterms  
 $m_1, m_3, m_9, m_{11}$

Gray code for rows & columns

AB \ CD	00	01	11	10
00	$m_0$	$m_1$	$m_3$	$m_2$
01	$m_4$	$m_5$	$m_7$	$m_6$
11	$m_{12}$	$m_{13}$	$m_{15}$	$m_{14}$
10	$m_8$	$m_9$	$m_{11}$	$m_{10}$

Plot 0's

$$m_1 \Rightarrow (AB=00, CD=01)$$

$$m_3 \Rightarrow (AB=00, CD=11)$$

$$m_9 \Rightarrow (AB=10, CD=01)$$

$$m_{11} \Rightarrow (AB=10, CD=11)$$

Grouping 0's

A varies  $(0 \leftrightarrow 1) \rightarrow$  eliminated

C varies  $(0 \leftrightarrow 1) \rightarrow$  eliminated

so simplified factor =  $B + D$

$$\therefore \boxed{F(A, B, C, D) = B + D}$$



### 3-variable K-map

- It has 8 cells ( $2^3$ )
- Gray code ordering ensures only 1 bit change between adjacent cells.

AB \ C	0	1		AB \ C	0 (C=0)	1 (C=1)
00	F <sub>0</sub>	F <sub>1</sub>		00	m <sub>0</sub>	m <sub>1</sub>
01	F <sub>2</sub>	F <sub>3</sub>	or	01	m <sub>2</sub>	m <sub>3</sub>
11	F <sub>6</sub>	F <sub>7</sub>		11	m <sub>6</sub>	m <sub>7</sub>
10	F <sub>4</sub>	F <sub>5</sub>		10	m <sub>4</sub>	m <sub>5</sub>

Minterms (SOP)	Maxterms (POS)
m <sub>0</sub> = A'B'C'	M <sub>0</sub> = A+B+C
m <sub>1</sub> = A'B'C	M <sub>1</sub> = A+B+C'
m <sub>2</sub> = A'BC'	M <sub>2</sub> = A+B'+C
m <sub>3</sub> = A'BC	M <sub>3</sub> = A+B'+C'
m <sub>4</sub> = AB'C'	M <sub>4</sub> = A'+B+C
m <sub>5</sub> = AB'C	M <sub>5</sub> = A'+B+C'
m <sub>6</sub> = ABC'	M <sub>6</sub> = A'+B'+C
m <sub>7</sub> = ABC	M <sub>7</sub> = A'+B'+C'

### SOP minimization (Using 1's)

Example  $F(A,B,C) = \sum (1,3,5,7)$

Step 1 → Plot 1's

place 1's at cells m<sub>1</sub>, m<sub>3</sub>, m<sub>5</sub>, m<sub>7</sub>

Step 2 → Grouping

(m<sub>1</sub>, m<sub>3</sub>) → vertical groups → A'C

(m<sub>5</sub>, m<sub>7</sub>) → vertical groups → AC

## 1) Sum of Products (SOP)

The SOP represents minterms in the Boolean Algebra.

SOP forms are OR-ed minterms (product terms)

It is a Boolean expression where each product term (or minterm) includes every variable of the function, either in its true or complemented form.

It represents the function as a sum of these minterms for which the output is 1.

Let learn how to write SOP form, with an example consider following truth table,

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

• identify '1's: The o/p Y is '1' for inputs  $\rightarrow (0,0,0), (0,1,1), (1,0,0), (1,1,0), \& (1,1,1)$

• write minterms  $\rightarrow (0,0,0) \rightarrow A'B'C', (0,1,1) \rightarrow A'BC$   
 $(1,0,0) \rightarrow AB'C', (1,1,0) \rightarrow ABC', (1,1,1) \rightarrow ABC$

• Sum the minterms  $\rightarrow$

$$Y = A'B'C' + A'BC + AB'C' + ABC' + ABC$$

$$m_0 = A'B'$$

$$m_2 = AB'$$

A/B	0	1
0	1	0
1	1	0

$$F(A, B) = m_0 + m_2$$

$$= A'B' + AB'$$

A changes from 0 to 1, B is constant = 0  
 $\therefore$  A is eliminated

$$\therefore F(A, B) = B'$$

POS minimization Example.

Problem

$$\text{Simplify } F(A, B) = \Pi(0, 2)$$

Step 1 Place 0's in k-map

$$0 = 0 \quad (A=0, B=0)$$

$$2 = 0 \quad (A=1, B=0)$$

$$m_0 = (A+B) \quad 00$$

$$m_1 = (A+B') \quad 01$$

$$m_2 = (A'+B) \quad 10$$

$$m_3 = (A'+B') \quad 11$$

$$F(A, B) = m_0 \cdot m_2$$

$$= (A+B) \cdot (A'+B')$$

$$= AA' + AB + A'B + BB$$

A/B	0	1
0	0	1
1	0	1

$$\text{but } AA' = 0, BB = B$$

$$F = AB + A'B + B$$

A changes to 0

B remains constant

$$\text{Absorption law } AB + B = B$$

$$\therefore F = B$$

$$\therefore F = B$$

eg.

A	B	$Y = \bar{A}B + A\bar{B}$
0	0	0
0	1	1
1	0	1
1	1	0

## Canonical Form

Canonical form refers to a standardized representation of a mathematical or computer science object that is unique within its equivalence class.

### Properties -

- Uniqueness - When two objects are equivalent, their canonical forms will be identical.
- Simplification - Converting an object to its canonical form often simplifies it, revealing its fundamental properties and making it easier to analyze.
- Standardization - Canonical forms provide a consistent, standard representation that eliminates ambiguity across various contexts.
- Equivalence - Canonical form is defined in the context of an equivalence relation, where all equivalent objects share the same unique canonical representation.

aidma There are two canonical forms are —

a) Sum of Products (SOP)

b) Product of Sum (POS)



miniterms  $\rightarrow$

$$m_0 = A'B'$$

$$m_1 = A'B$$

$$m_2 = AB'$$

$$m_3 = AB$$

### • SOP Minimization Example

1) Problem.

Simplify  $F(A,B) = \sum (1,3)$

Step 1. Place 1's in k-map

$$m_1 = 1 \quad (A=0, B=1)$$

$$m_3 = 1 \quad (A=1, B=1)$$

$$F(A,B) = m_1 + m_3 \\ = A'B + AB$$

A \ B	0	1
0	0	1
1	0	1

Step 2. Group adjacent 1's

•  $m_1$  and  $m_3$  form a vertical group

Step 3. Write simplified expression

In this group,  $B=1$  is constant,  $A$  changes (0  $\rightarrow$  1) so it is eliminated,  $B$  is constant = 1

$$\therefore \boxed{F(A,B) = B}$$

2)  $F(A,B) = \sum (0,2)$

$$m_0 = 1 \quad (A=0, B=0)$$

$$m_2 = 1 \quad (A=1, B=0)$$

$$F(A,B) = m_0 + m_2$$

$$= A'B' + AB'$$

Step 3- Expression

$$F = A'C + AC = C$$

$$\therefore \text{Answer} \boxed{F = C}$$

POS minimization (Using 0's)

Solve

$$F(A, B, C) = \Pi(0, 2, 4, 6)$$

Step 1 Plot 0's

Place 0 at  $m_0, m_2, m_4, m_6$

Step 2 Grouping

$(m_0, m_2) \rightarrow$  vertical group  $\rightarrow (A+C)$

$(m_4, m_6) \rightarrow$  vertical group  $\rightarrow (A'+C)$

expression

$$F = (A+C) \cdot (A'+C)$$

$$F = C$$

$$\boxed{\text{Answer} \rightarrow F = C}$$